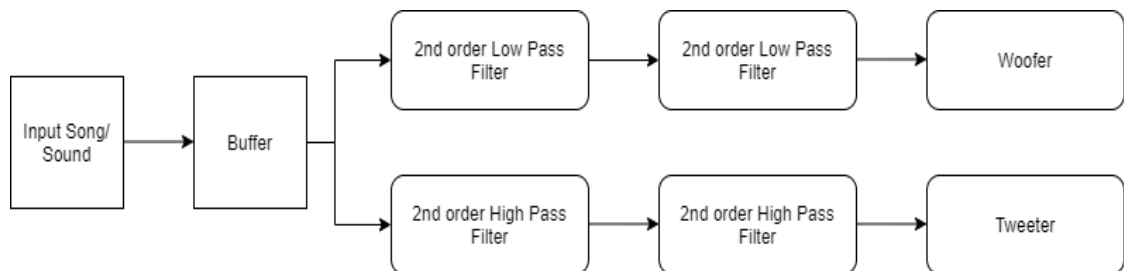


# 2-Way Crossover Filter


Govind J S(b180544ec), G Arunteja Reddy(b180679ec),  
Gedela Akhil (b180609ec), G Santosh Babu(b180326ec)

1. **Aim of the project:** To design and implement a 2-way cross over filter
2. **Block diagram:**




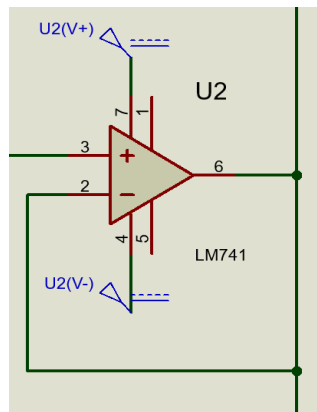3. **Design:**

Buffer Circuit: The buffer circuit is simply a voltage follower to increase the current gain.



4<sup>th</sup> order low pass filter:

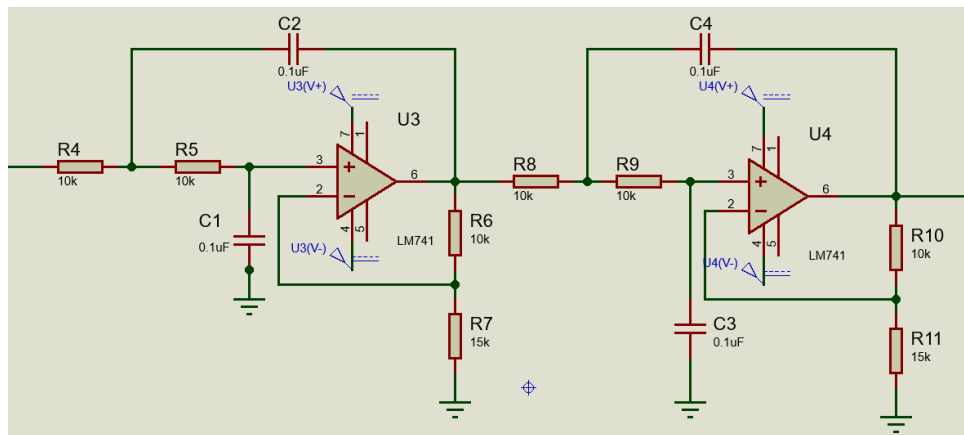

Desired Cut-off Frequency = 160 Hz


Cut-off frequency of LPF=  $1/2\pi RC$

Assume C = 0.1uF

Doing necessary calculations, we get R = 10k

Now we cascaded two 2<sup>nd</sup> order filters to generate a 4<sup>th</sup> order LPF with higher gain value.

4<sup>th</sup> order high pass filter:

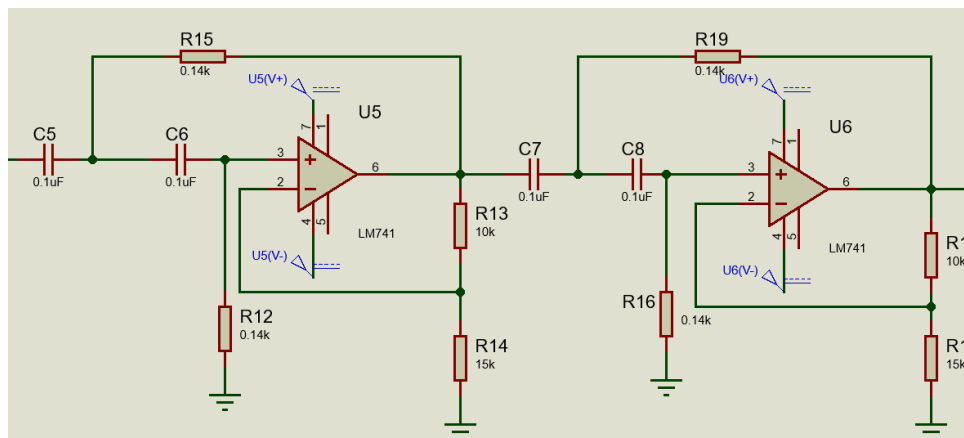

Desired Cut-off Frequency = 11kHz

Cut-off frequency of LPF=  $1/2\pi RC$

Assume  $C = 0.1\mu F$


Doing necessary calculations, we get  $R = 0.14k$

Now we cascaded two 2<sup>nd</sup> order filters to generate a 4<sup>th</sup> order LPF with higher gain value.

#### 4. Simulation Results

a.

Voltage Follower:

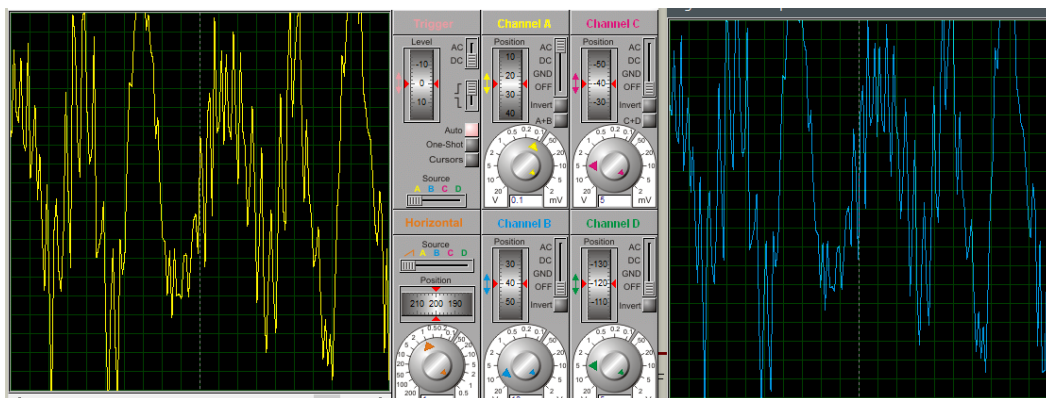


Input

Output

Scale: On Y Axis 1 division = 0.1V

On X axis 1 division = 1ms

2<sup>nd</sup> order Low pass filter

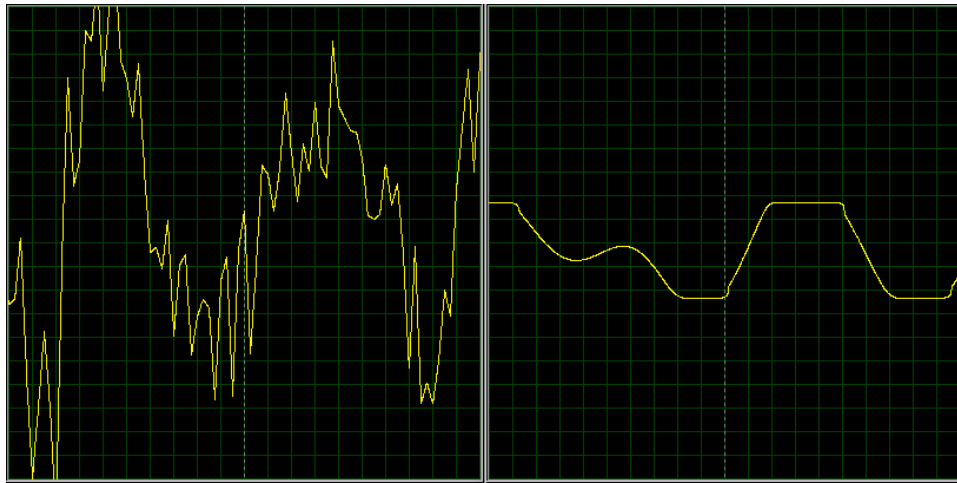


Input

Output

Scale: On Y Axis 1 division = 0.1V

On X axis 1 division = 0.1ms

2<sup>nd</sup> order High pass filter

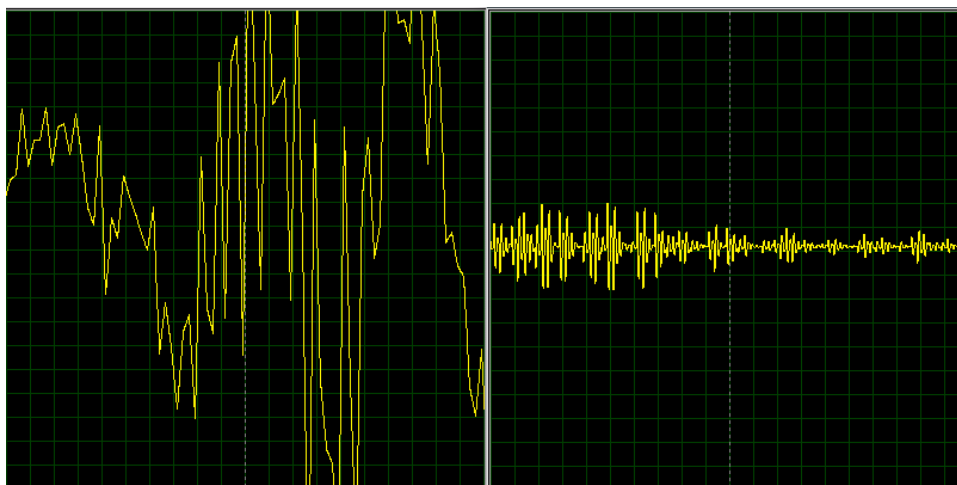


Input

Output

Scale: On Y Axis 1 division = 0.1V

On X axis 1 division = 0.1ms

b.

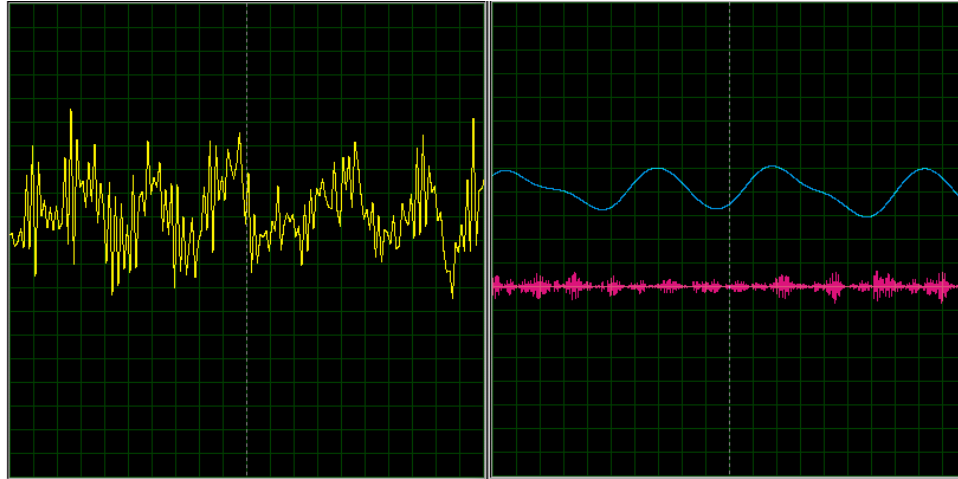

Overall input

Overall output

Woofer (LPF) output: Blue

Tweeter (HPF): Pink

Scale: On Y Axis 1 division = 0.1V

On X axis 1 division = 0.1ms

## 5. Results

A proper 2-way active crossover filter was designed by using relevant equations and implemented in a simulation. The simulation was given input audio and output was obtained in two separate speakers within simulation separated by a specific frequency.

